

**Physics 2401 Summer 2, 2008
Exam II**

$e = 1.60 \times 10^{-19} \text{ C}$, $m(\text{electron}) = 9.11 \times 10^{-31} \text{ kg}$, $\epsilon_0 = 8.845 \times 10^{-12} \text{ C}^2/\text{Nm}^2$,
 $k_e = 9.0 \times 10^9 \text{ Nm}^2/\text{C}^2$, $m(\text{proton}) = 1.67 \times 10^{-27} \text{ kg}$. $n = \text{nano} = 10^{-9}$, $\mu = \text{micro} = 10^{-6}$, $m = \text{milli} = 10^{-3}$
 Put your answers on the orange scantron which you brought. There is only one correct answer for each questions. All questions are weighted equally.

1. A $30\text{-}\mu\text{F}$ capacitor is charged to 80 V and then connected across an initially uncharged capacitor of unknown capacitance C . If the final potential difference across the $30\text{-}\mu\text{F}$ capacitor is 20 V , determine C .

- a. $60 \mu\text{F}$
 b. $75 \mu\text{F}$
 c. $45 \mu\text{F}$
 d. $90 \mu\text{F}$
 e. $24 \mu\text{F}$

$Q_{\text{tot}} = C_1(80\text{V}) = 2.4 \mu\text{C}$
 Divides to Q_1, Q_2 such that final $V_1 = V_2$
 or $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} = 20\text{V}$ Also $Q_1 + Q_2 = Q_{\text{tot}}$
 $Q_1 = C_1(20\text{V}) = 0.60 \mu\text{C}$ so $Q_2 = 1.8 \mu\text{C} = C_2(20\text{V})$
 $C_2 = 90 \mu\text{F}$

2. A parallel plate capacitor of capacitance C_0 has plates of area A with separation d between them. When it is connected to a battery of voltage V_0 , it has charge of magnitude Q_0 on its plates. It is then disconnected from the battery and the plates are pulled apart to a separation $2d$ without discharging them. After the plates are $2d$ apart, the magnitude of the charge on the plates and the potential difference between them are

- a. $\frac{1}{2}Q_0, \frac{1}{2}V_0$
 b. $Q_0, \frac{1}{2}V_0$
 c. Q_0, V_0
 d. $Q_0, 2V_0$
 e. $2Q_0, 2V_0$


Q constant. So $\epsilon = \epsilon_0 E$ also constant.
 $V' = 2V_0$ since $V = Ed$
 and $d' = 2d$

3. A parallel plate capacitor is connected to a battery and charged. It remains connected to the battery as a piece of dielectric material with dielectric constant K is inserted between the plates. When the material is inserted, the stored energy in the capacitor

- a) stays the same b) increases c) decreases

$U = \frac{1}{2} CV^2 = \frac{1}{2} K C_0 V^2 \quad (K > 1)$

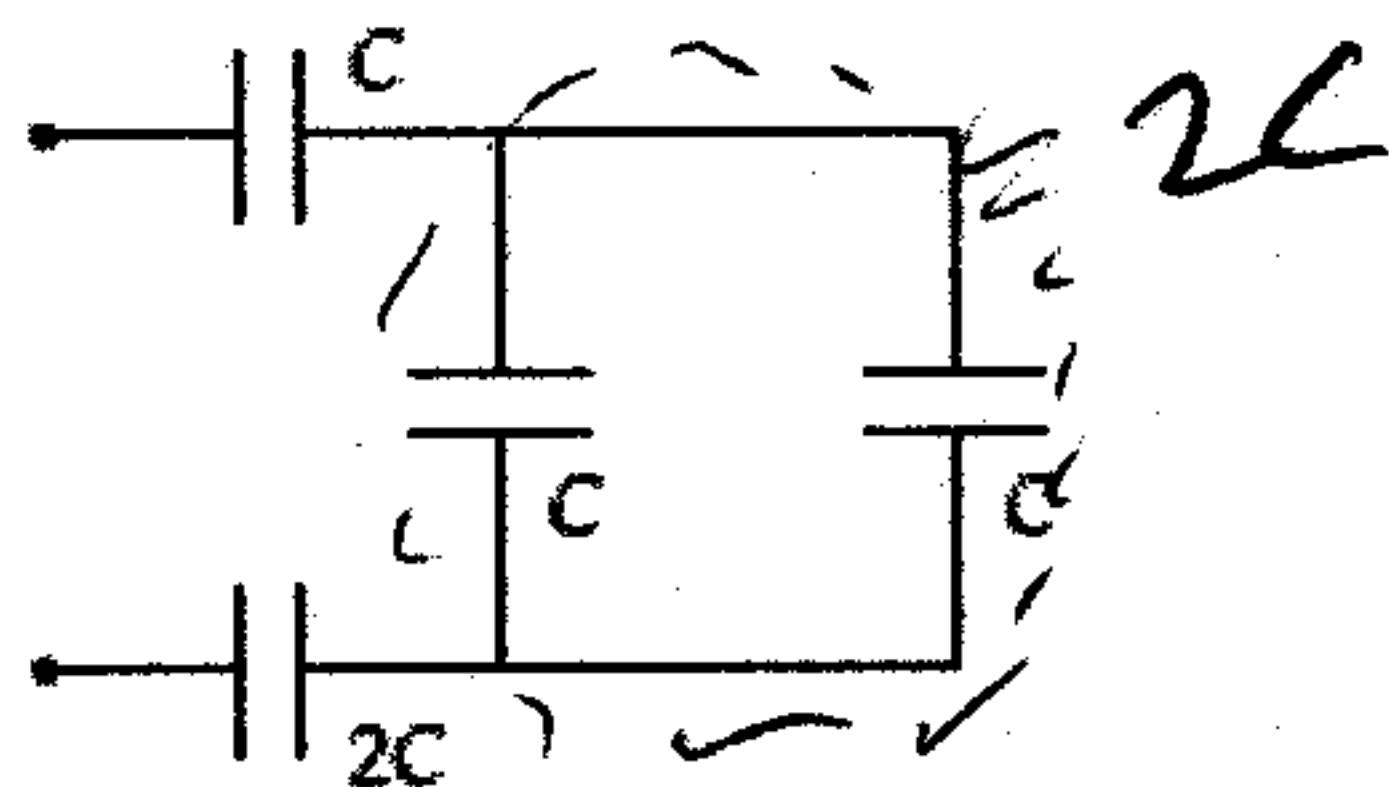4. Determine the equivalent capacitance of the combination shown when $C = 12 \text{ pF}$.



$C_{\text{eq}} = \left(\frac{1}{C} + \frac{1}{2C} + \frac{1}{2C} \right)^{-1} = \left(\frac{2}{C} \right)^{-1} = C/2$

- a. 48 pF
 b. 12 pF
 c. 24 pF
 d. 6.0 pF
 e. 59 pF