


11. A resistor of unknown resistance and a  $15\text{-}\Omega$  resistor are connected across a  $20\text{-V}$  emf in such a way that a  $2.0\text{ A}$  current is observed in the emf. What is the value of the unknown resistance?

- a.  $75\text{ }\Omega$   
b.  $12\text{ }\Omega$   
c.  $7.5\text{ }\Omega$   
d.  $30\text{ }\Omega$   
e.  $5.0\text{ }\Omega$

$$R_{eq} = \frac{20V}{2.0A} = 10\Omega < 15\Omega \text{ so must be parallel}$$

$$\frac{1}{10\Omega} = \frac{1}{15\Omega} + \frac{1}{R_u} \quad \frac{1}{R_u} = 0.033 \frac{1}{\Omega} \quad R_u = 30\Omega$$

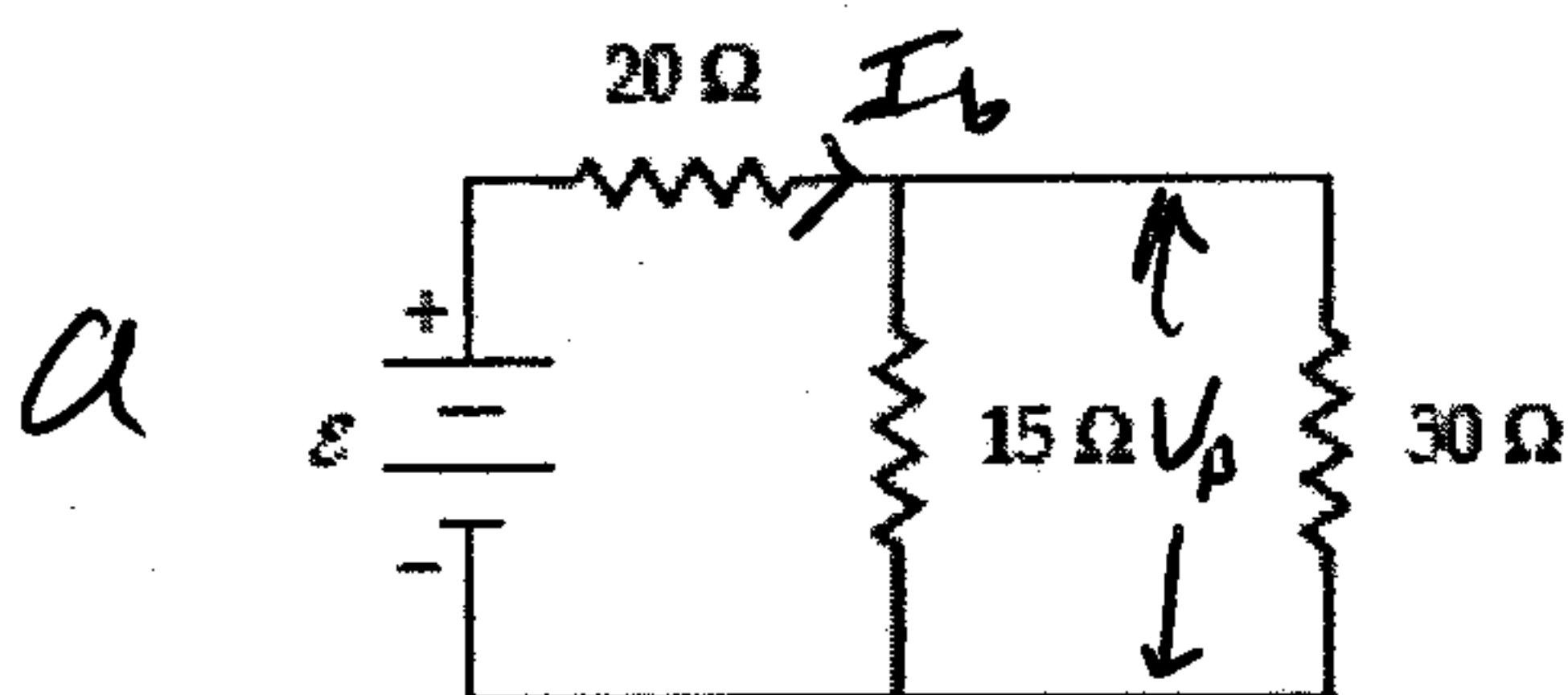12. What is the current in the  $15\text{-}\Omega$  resistor when  $\epsilon = 9.0\text{ V}$ ?



$$R_{eq} = \left( \frac{1}{15} + \frac{1}{30} \right)^{-1} \Omega + 20\Omega = 30\Omega$$


$$I_b = \frac{\epsilon}{R_{eq}} = 0.30\text{ A}$$

$$V_p = \epsilon - I_b(20\Omega) = 3.0\text{ V}$$

$$I_{15} = \frac{V_p}{15\Omega} = 0.20\text{ A}$$

- a.  $0.20\text{ A}$   
b.  $0.30\text{ A}$   
c.  $0.10\text{ A}$   
d.  $0.26\text{ A}$   
e.  $0.60\text{ A}$

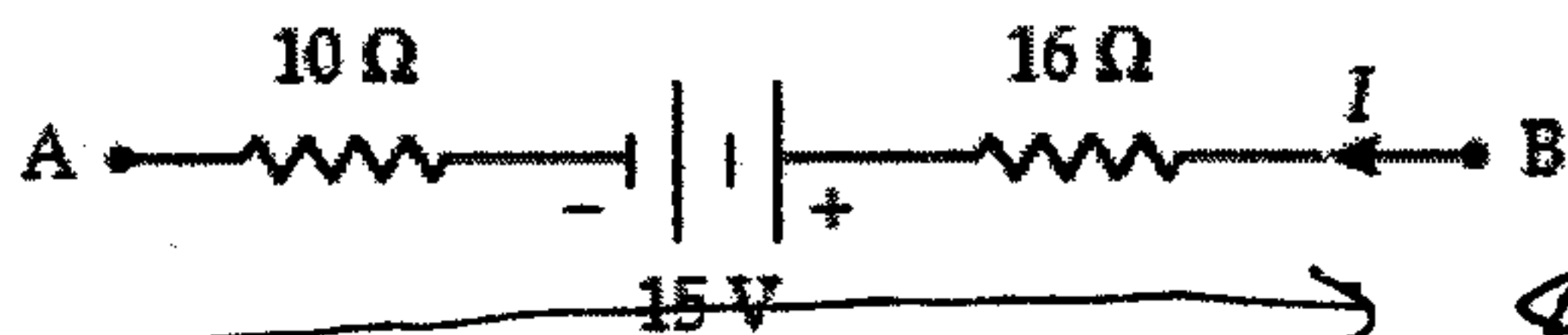13. What is the potential difference  $V_B - V_A$  when  $I = 0.50\text{ A}$  in the circuit segment shown below?



add ΔV's this way

$$\Delta V = (10\Omega)I + 15V + (16\Omega)I = 28V$$

- a.  $+28\text{ V}$   
b.  $+2.0\text{ V}$   
c.  $-28\text{ V}$   
d.  $-2.0\text{ V}$   
e.  $+18\text{ V}$

14. A capacitor in a single-loop RC circuit is charged to 85% of its final potential difference in  $2.4\text{ s}$ . What is the time constant for this circuit?

- a.  $1.5\text{ s}$   
b.  $1.3\text{ s}$   
c.  $1.7\text{ s}$   
d.  $1.9\text{ s}$   
e.  $2.9\text{ s}$

$$V = \frac{Q}{C} = V_f (1 - e^{-t/RC})$$

$$0.85 = 1 - e^{-t/RC} \quad e^{-t/RC} = 0.15$$

$$-t/RC = \ln(0.15) \quad RC = \frac{-2.4\text{ s}}{\ln(0.15)} = 1.3\text{ s}$$

15. If  $480\text{ C}$  pass through a  $4.0\text{-}\Omega$  resistor in  $10\text{ min}$ , what is the potential difference across the resistor?

- a.  $3.6\text{ V}$   
b.  $2.8\text{ V}$   
c.  $2.4\text{ V}$   
d.  $3.2\text{ V}$   
e.  $5.0\text{ V}$

$$I = \frac{\Delta Q}{\Delta t} = \frac{480\text{ C}}{(10\text{ min})(60\text{ s/min})} = 0.80\text{ A}$$

$$V = IR = 3.2\text{ V}$$