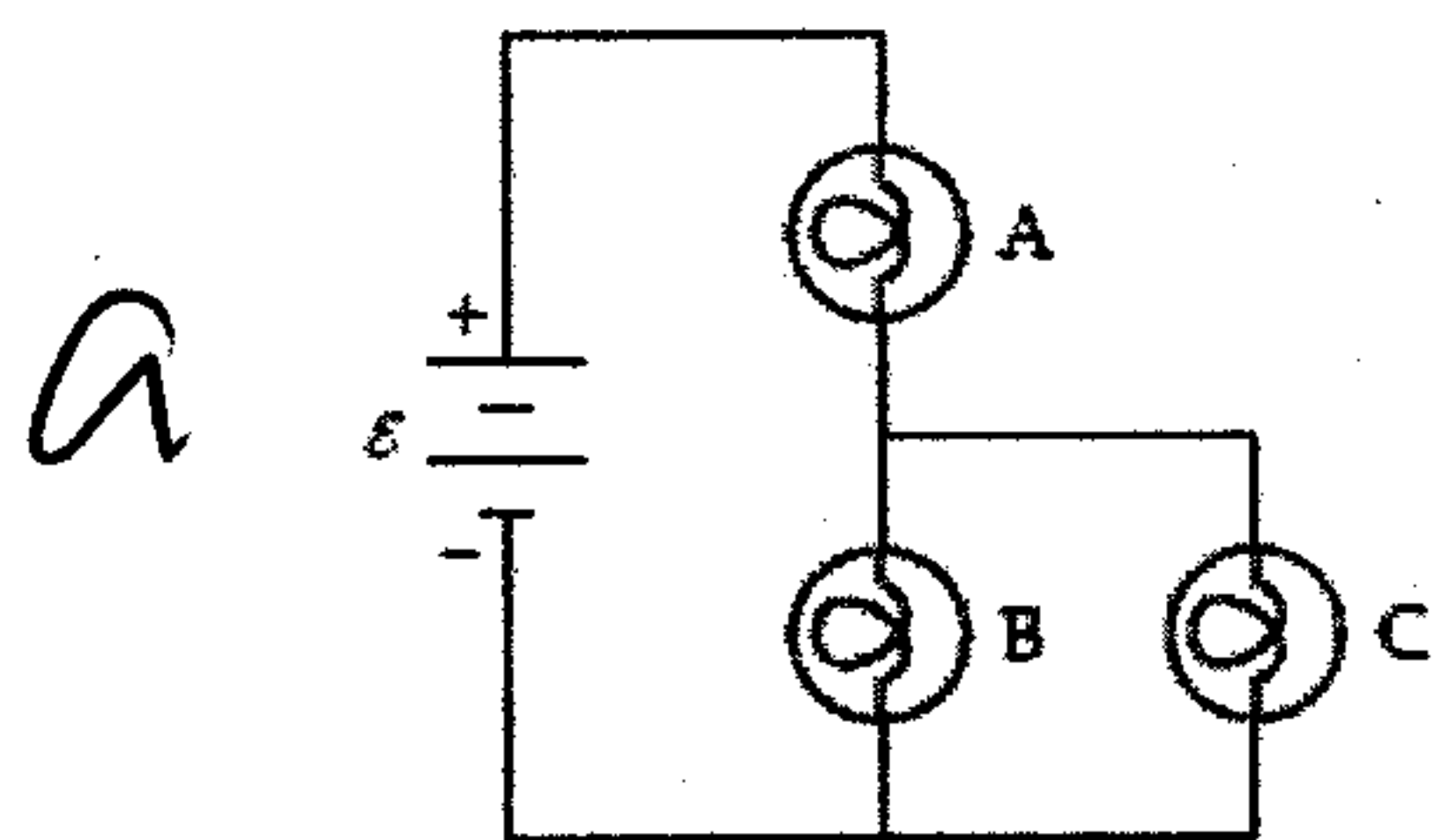


- b 16. A fully charged capacitor acts like
 a) a resistanceless wire (short circuit) **b) an infinite resistance (open circuit)**

17. In a loop in a closed circuit, the sum of the currents entering a junction equals the sum of the currents leaving a junction because

- e
 a. the potential of the nearest battery is the potential at the junction.
 b. there are no transformations of energy from one type to another in a circuit loop.
 c. capacitors tend to maintain current through them at a constant value.
 d. current is used up after it leaves a junction.
e) charge is neither created nor destroyed at a junction.

18. The circuit below contains three 100 watt light bulbs. The emf $\epsilon = 110$ V. Which light bulb(s) is(are) the brightest?




Full battery current passes through A, so P_A is greatest.

- a) A
 b. B
 c. C
 d. B and C
e. All three are equally bright.

19. A voltmeter

- d
 a) should be connected in series and have a small internal resistance
 b) should be connected in parallel and have a small internal resistance
 c) should be connected in series and have a large internal resistance
d) should be connected in parallel and have a large internal resistance

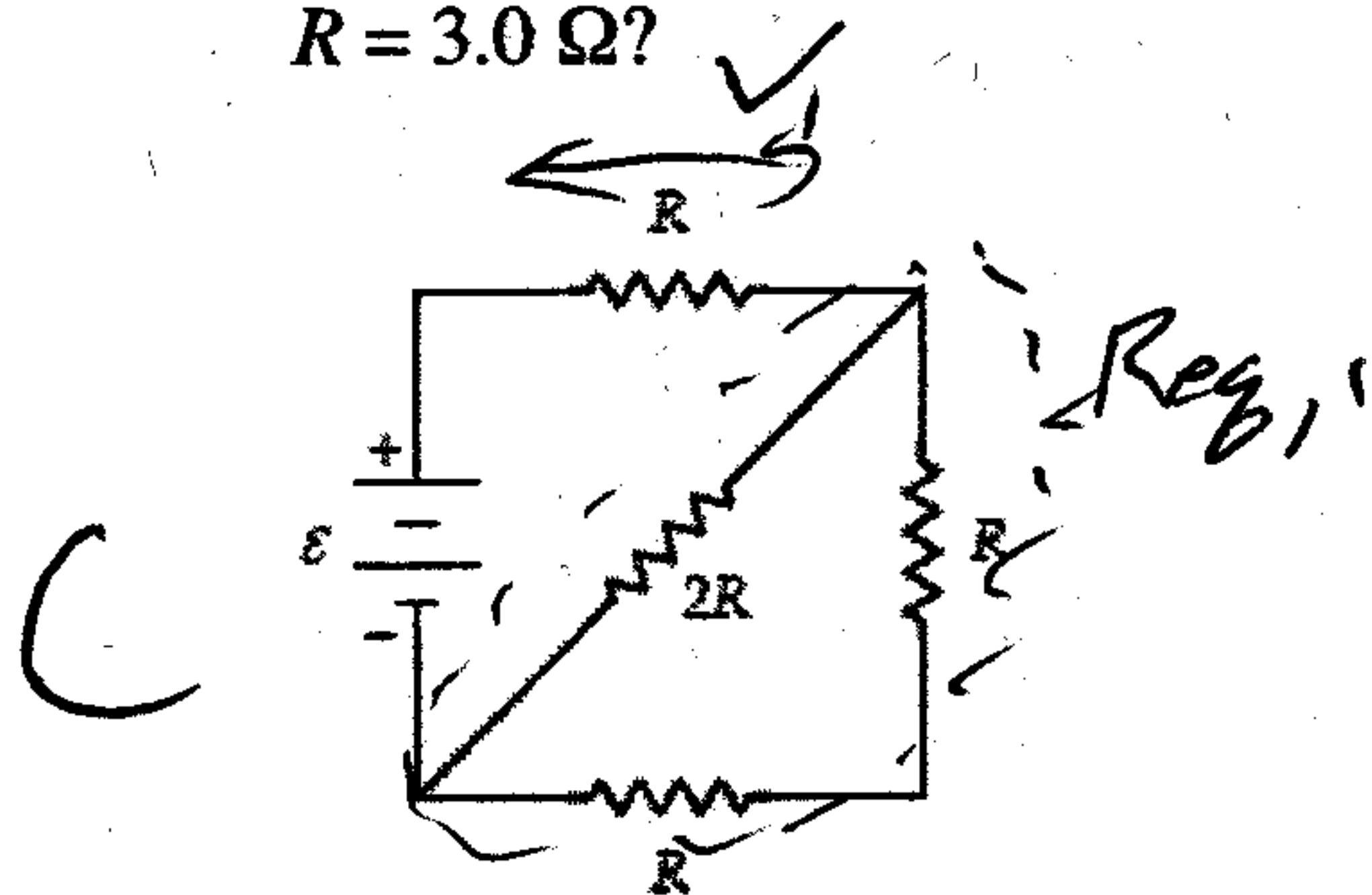20. At what rate is thermal energy being generated in the $2R$ -resistor when $\epsilon = 12$ V and $R = 3.0 \Omega$?



- a. 12 W
 b. 24 W
c) 6.0 W
 d. 3.0 W
 e. 1.5 W

$$\frac{1}{R_{eq1}} = \left(\frac{1}{2R} + \frac{1}{R+R} \right)$$

$$R_{eq1} = R$$

$$R_{eq} = R + R = 2R$$

$$I = \frac{\epsilon}{R_{eq}} = \frac{\epsilon}{2R} = \frac{12V}{6\Omega} = 2.0A$$

$$V_{2R} = \epsilon - V_1 = 12V - (2.0A)(3.0\Omega) = 6V$$

$$P_{2R} = \frac{V_{2R}^2}{2R} = \frac{(6V)^2}{6.0\Omega} = 6W$$